




Phase 2, project 1: Single Cycle MIPS processor

Copyrights of the manual are reserved for IEEE CUSB 2022.

Introduction:

You are required to implement a 32-bit single-cycle microarchitecture MIPS processor. The single cycle executes an entire instruction in one cycle. In other words, instruction fetch, instruction decode, execute, write back, and program counter update occurs within a single clock cycle.

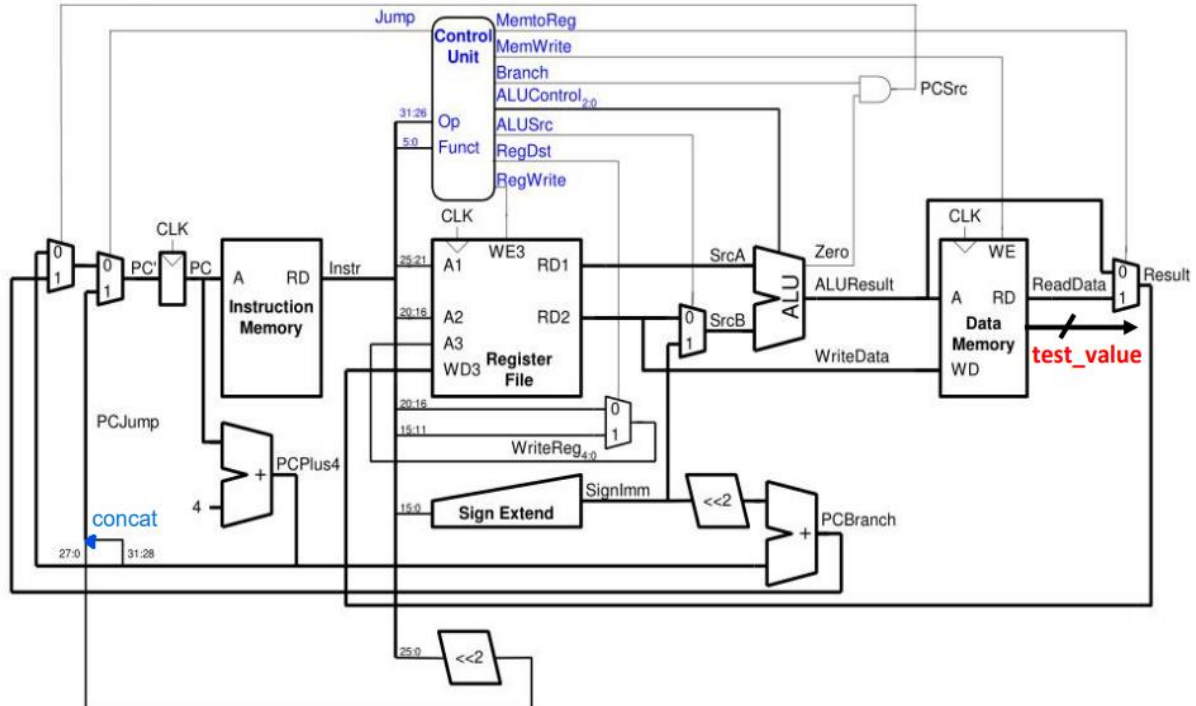
The objective is to write the RTL Verilog files for all sub-modules of the MIPS processor (Instruction memory, data memory, ALU, etc.) then implementing the top module of MIPS processor.



Complete single-cycle MIPS processor. (from David M. Harris, Sarah L. Harris - Digital Design and Computer Architecture)

Top module view:

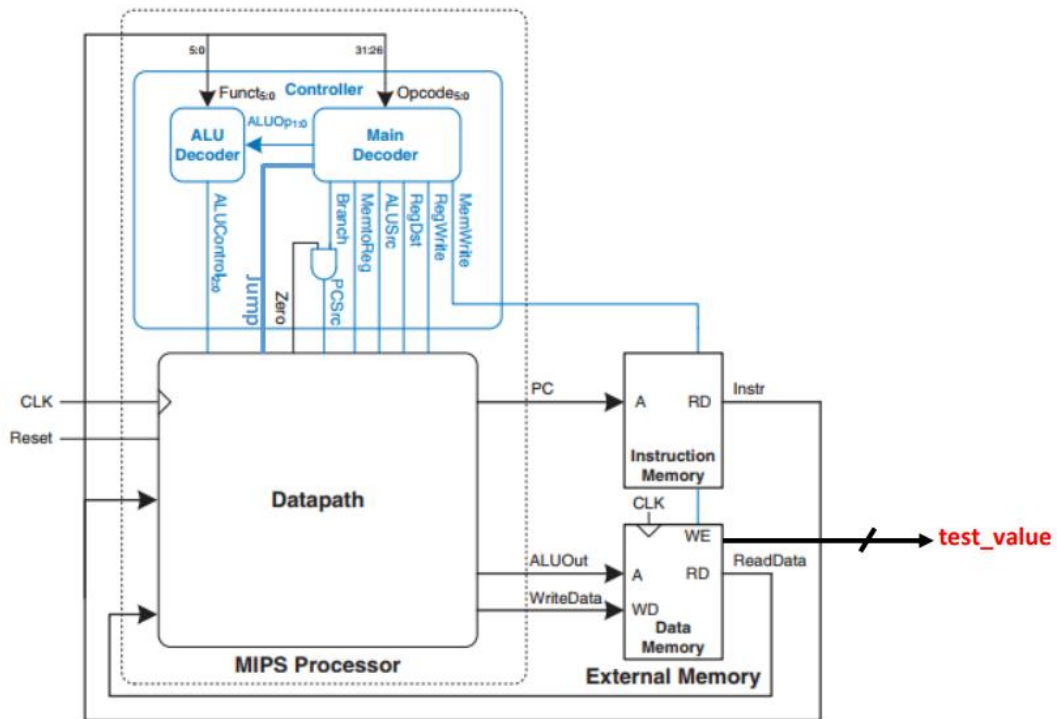The processor is composed of The processor is composed of a datapath and a controller. The controller, in turn, is composed of the main decoder and the ALU decoder. Here is a block diagram of interfacing with external memories.



MIPS single-cycle processor interfaced to external memory. (from David M. Harris, Sarah L. Harris - Digital Design and Computer Architecture)

Main modules:

1- ALU: The ALU forms the heart of most computer systems. The 3-bit ALUControl signal specifies the operation. The ALU generates 32-bit ALUResult and a zero flag to indicate if result == 0.


ALUControl	Function
000	Bitwise AND
001	Bitwise OR
010	Addition
011	Not used
100	Subtraction
101	Multiplication

110	Set less than (alurest = 1 if srca < srcb)
111	Not used

2- Program counter: program counter register contains the 32-bit address to execute. The PC is updated at the rising edge of clk and cleared whenever the active low reset is asserted asynchronously.


3- Instruction memory: PC is connected to the address input of the instruction memory. The instruction memory fetches the 32-bit instruction. It is a ROM that holds the program that your CPU will execute. This ROM has width = 32 bits and depth = 256 entries (1KB ROM), i.e, you will only connect bits 9 to 2 in the address bus as it is byte aligned. Instructions are read asynchronously.

4- Register File: The Register file contains the 32 32-bit MIPS registers. The register file has two read output ports (RD1 and RD2) and a single input write port (WD3). The register file is **read asynchronously and written synchronously at the rising edge of the clock**. The register file supports simultaneous reads and writes. The register file has width = 32 bits and depth = 32 entries. Note that there is a write enable signal that is used to enable writing the new value on the data bus (WD3) to the specified register address (A3).

 

5- Data memory: It is a RAM that provides a store for the CPU to load from and store to. **Reads are asynchronous and writes are synchronous** to the rising edge of the clk signal. It is the same width and depth of instruction memory. Note that test_value is read from address 0x0000_0000 (first

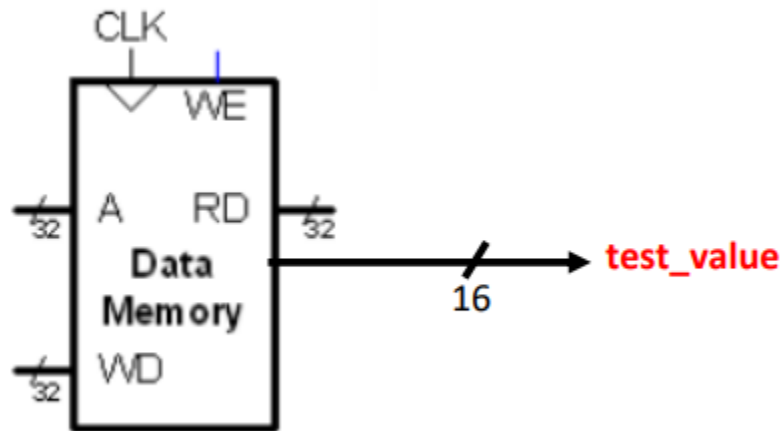location on memory) the least 16 significant bits. This is for testing purposes only.




6- Control unit: the control unit computes the control signals based on the opcode and funct fields of the instruction, **instr_{31:26}** and **instr_{5:0}**. Most of the control information comes from the opcode, but R-type instructions also use the funct field to determine the ALU operation. Thus, we will simplify that by factoring control unit into two blocks: **ALU decoder** and **main decoder**.

ALU decoder truth table:

ALUOp	funct	ALUControl
00	xxxxxx	010
01	xxxxxx	100
10	add = 6'b10_0000	010
	sub = 6'b10_0010	100
	slt = 6'b10_1010	110
	mul = 6'b01_1100	101
Default	xxxxxx	010

opcode	jump	aluop	memwrite	regwrite	regdest	alusrc	memtoreg	branch
lw = 6'b10_0011	0	00	0	1	0	1	1	0
sw = 6'b10_1011	0	00	1	0	0	1	1	0
R type = 6'b00_0000	0	10	0	1	1	0	0	0
addi = 6'b00_1000	0	00	0	1	0	1	0	0
beq = 6'b00_0100	0	01	0	0	0	0	0	1
Jal& j = 6'b00_0010	1	00	0	0	0	0	0	0
Default	0	00	0	0	0	0	0	0

Main decoder truth table:

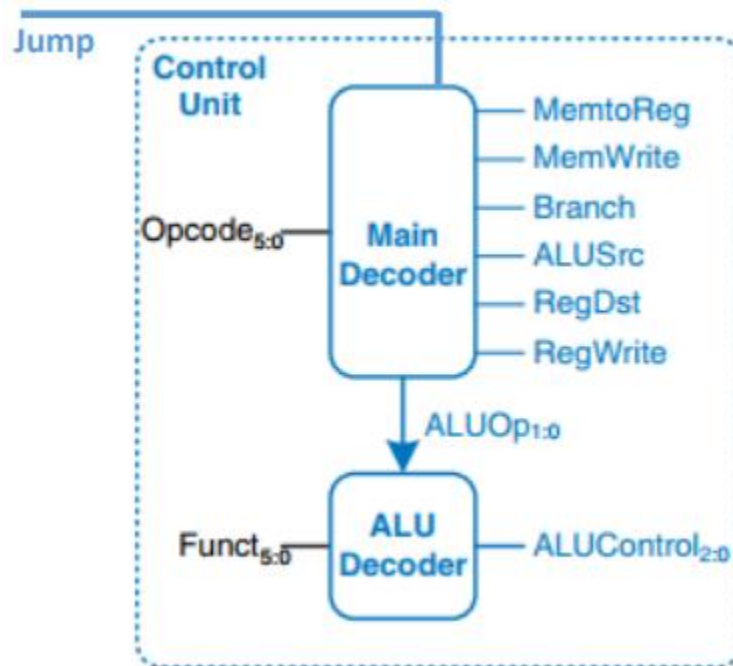

Small modules:

1. **Sign Extend:** Sign extension copies the MSB of a short input (16 bits) into all the upper bits of the longer output (32 bits).
2. **Shift_left_twice:** you need to make this block parametrized to use in two different versions of data input width.
3. **Adder**
4. **MUX:** you are also required to make a parametrized 2x1 mux.

Testing programs machine codes:

1- Number Factorial: (hex format)

```
00008020
20100007    // change the least two significant decimals with the number
00008820
20110001
12000003
0230881C
2210FFFF
08000004
AC110000
```


2- Greatest Common Divisor: (hex format)

```
00008020
20100078    // change the least two significant decimals with the number
00008820
201100B4    // change the least two significant decimals with the number.
00009020
12110006
0211482A
11200002
02308822
08000005
02118022
08000005
00109020
AC120000
```


These programs you need to compile and load it onto the instruction memory and reset your processor to start executing from memory location 0000 0000h.

Examples of simulation:

1- Factorial of 7:

 

2- GCD of 120 and 180

 

Details of submission:

- [individual] you need to submit a pdf that contains codes and simulation on canvas.
- Due date: 5/10/2023, 11:59 PM